

Introduction to Digital Computing Theory
Homework # 4 - Boolean Algebra and DeMorgan's Theorem


Student's Name _____

Instructions:

- Show all work to receive full credit
-

Boolean Analysis of Logic Circuits

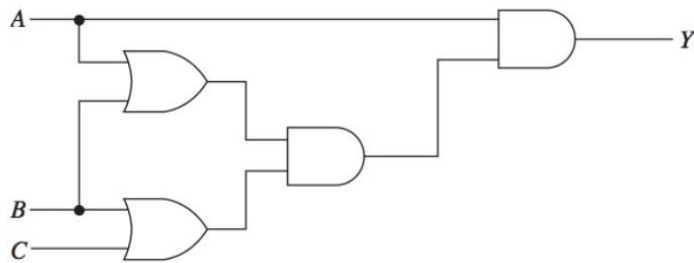
Question 1) Find the output and use Boolean algebra to simplify the output. Also sketch the simplified circuit.



- Output Y _____
- Simplified output Y _____
- Draw the simplified circuit


Question 2 and 3) Find the output X and use Boolean algebra and DeMorgan's theorem to simplify the output. Also sketch the simplified circuit.

2.

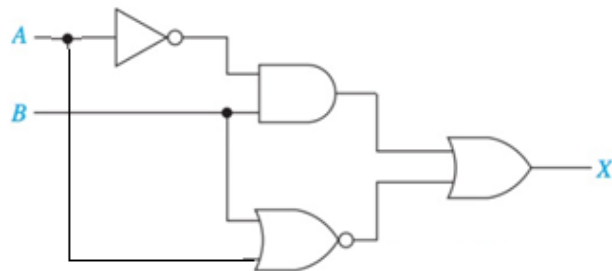

- Output X _____
- Simplified output X _____
- Draw the simplified circuit

3.

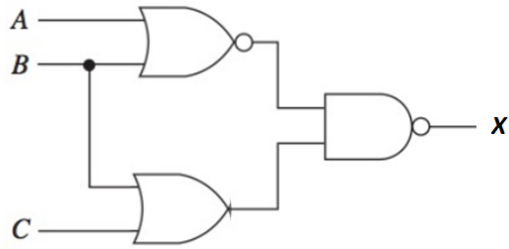

- Output X _____
- Simplified output X _____
- Draw the simplified circuit

Question 4) Simplify the following output using Boolean algebra and/or DeMorgan's techniques

- $X = AB + (\bar{B} + C)\bar{A} + A\bar{B}$
- $Z = \bar{A}B + \bar{A}\bar{B}C + \bar{B}\bar{C} + \bar{B}C$
- $W = \overline{(\bar{\bar{A}} + B)BC} + \bar{B}C$
- $Y = \overline{(A + \bar{B})(\bar{C} + D)}$

-----Homework 4 Ends Here -----