

Introduction to Digital Computing


Homework 7 – SR, D, and JK flip flops

Student's Name: _____


Instruction:

- Show all work to receive full credit. Box or circle the answer
- The following exercises are for theory practices, some of them have no real application.

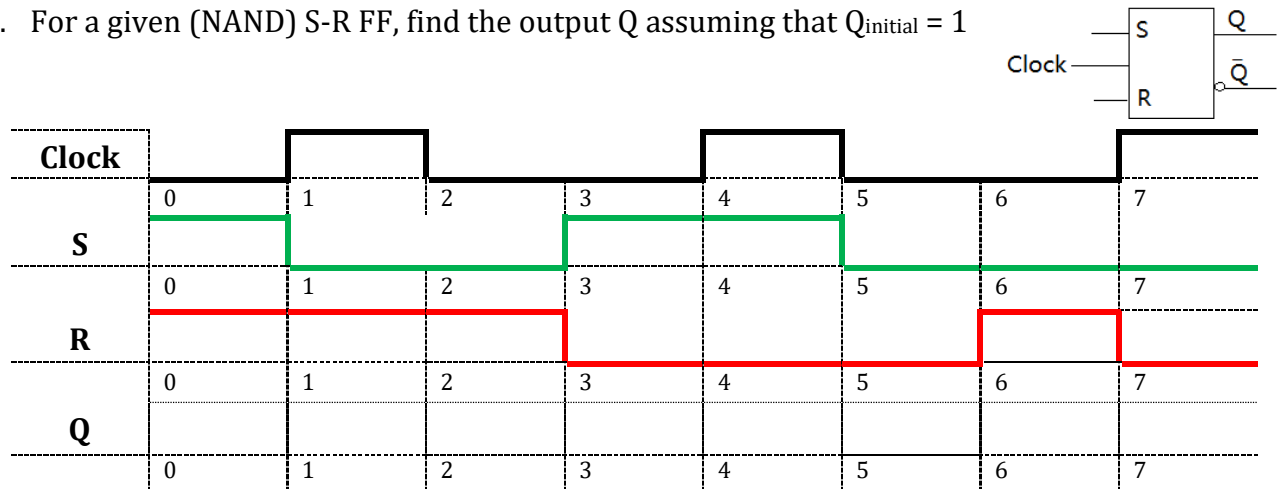
1. For a given (NAND) S-R FF, find the output Q assuming that $Q_{\text{initial}} = 1$



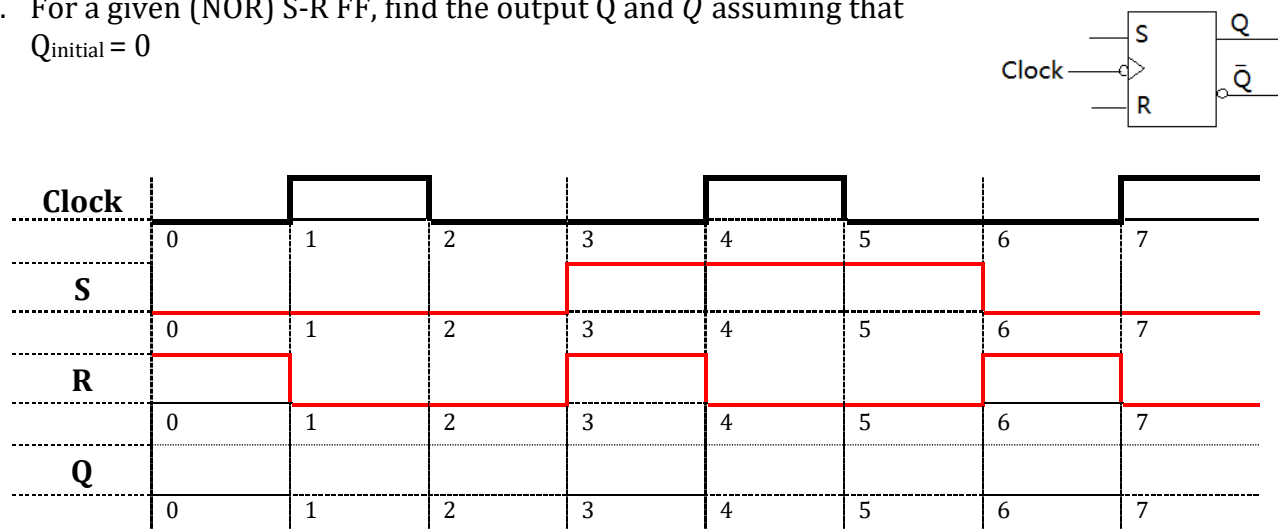
2. For a given (NOR) S-R FF, find the output Q and \bar{Q} assuming that $Q_{\text{initial}} = 0$



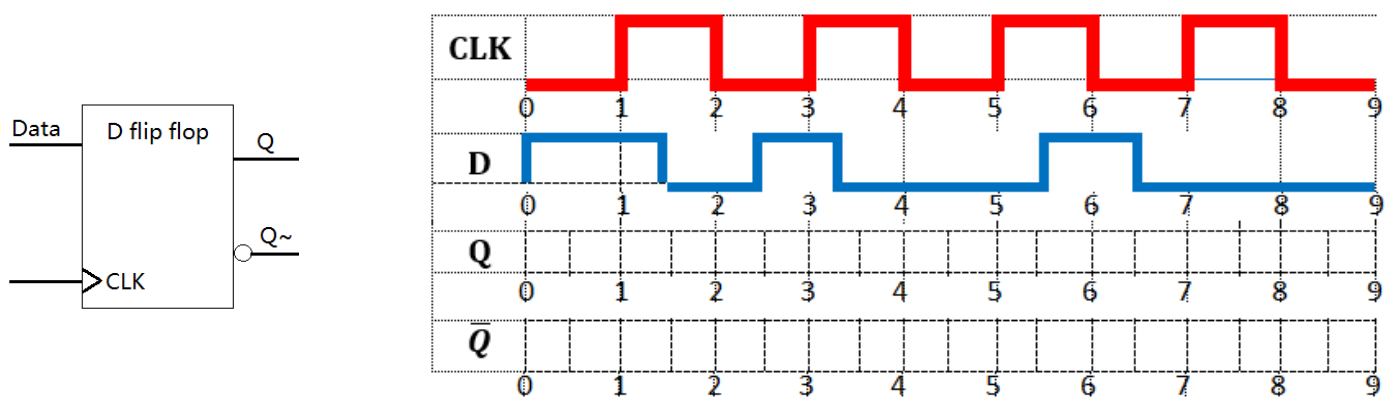
3. For the following D-flip flop circuit, sketch output Q and \bar{Q} if Q_{initial} is 0



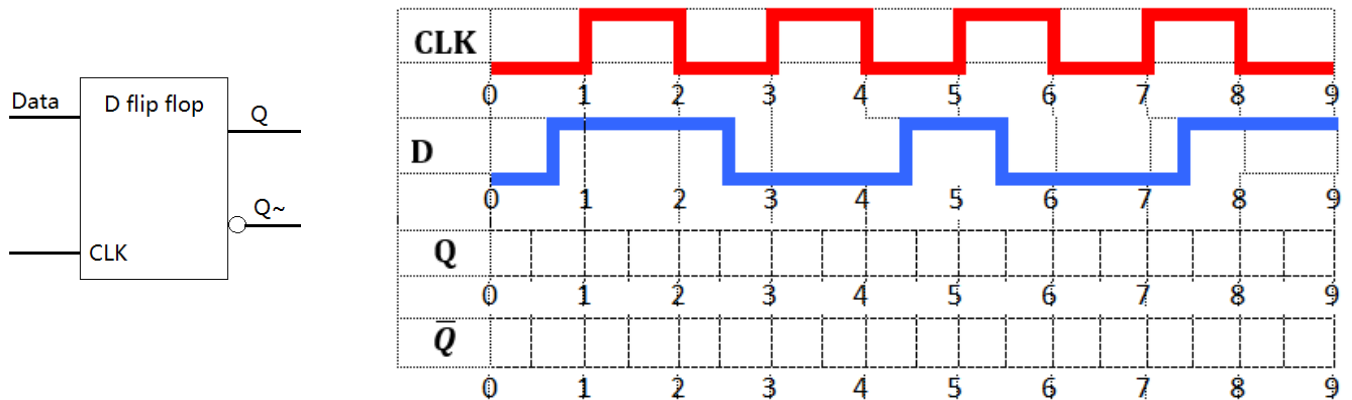4. For the following D-flip flop circuit, sketch output Q and \bar{Q} if Q_{initial} is 1



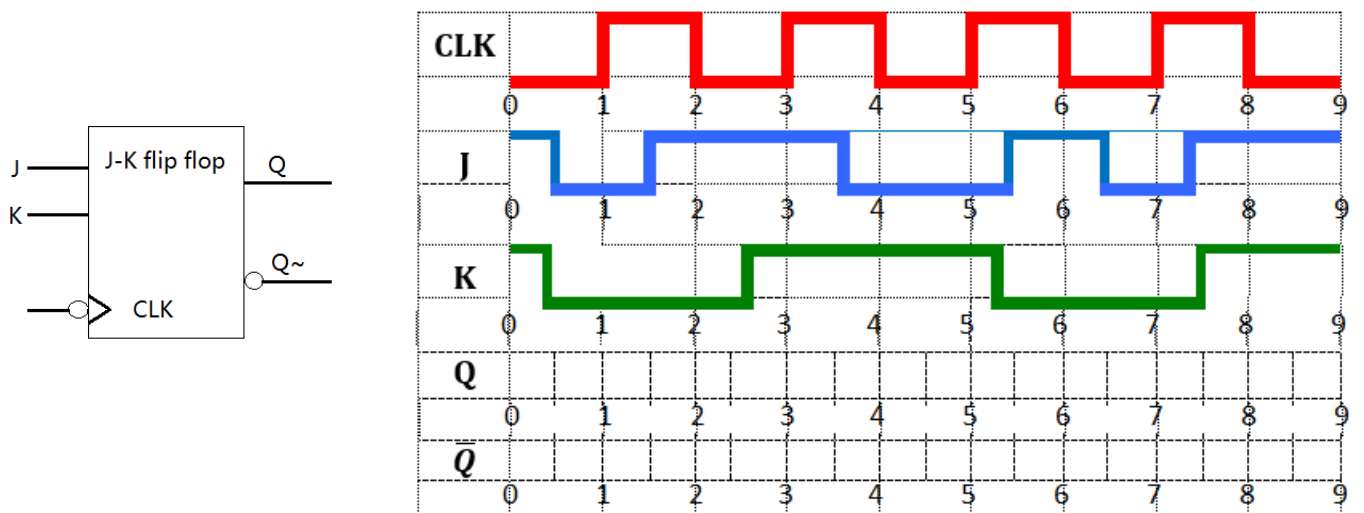5. For the following J-K flip flop circuit, sketch output Q and $Q\sim$ if Q_{initial} is 1



6. For the following J-K flip flop circuit, sketch output Q and $Q\sim$ if Q_{initial} is 0

